

# ELC 2137 Lab 5: Intro to Verilog

Celaine Hornsby

September 29, 2020

## Summary

In this lab we learned how to code the circuits that we built in previous labs. We were able to code the half adder, full adder, and 2-bit adder subtractor that we built in lab. We gained a better understanding of how Verilog and Vivado works from this lab. through the use of design files and simulation files that acted as a test bench for our design files.

## Q&A

1. What is one thing that you still don't understand about Verilog?

I don't understand how to run simulations of design files. Mine constantly have confusing errors that make my simulations not be able to run.

## Code

Listing 1: halfadder.sv

```
'timescale 1ns / 1ps
//
// //////////////////////////////////////
//
// Company: ELC 2137
// Engineer: Celaine Hornsby
//
// Create Date: 09/24/2020 04:47:49 PM
// Design Name:
// Module Name: halfadder
// Project Name:
// Target Devices:
// Tool Versions:
// Description:
//
// Dependencies:
//
// Revision:
// Revision 0.01 - File Created
// Additional Comments:
//
```



```

        initial begin
            a1 = 0; b1 = 0; #10;
            a1 = 1; b1 = 0; #10;
            a1 = 0; b1 = 1; #10;
            a1 = 1; b1 = 1; #10;
            $finish ;
        end
    endmodule

```

---

Listing 3: fulladder.sv

---

```

`timescale 1ns / 1ps
//
//
// Company: ELC 2137
// Engineer: Celaine Hornsby
//
// Create Date: 09/24/2020 05:07:41 PM
// Design Name:
// Module Name: fulladder
// Project Name:
// Target Devices:
// Tool Versions:
// Description:
//
// Dependencies:
//
// Revision:
// Revision 0.01 - File Created
// Additional Comments:
//
//
//
module fulladder(
    input ain,
    input bin,
    input cin,
    output cout,
    output sout
);

    wire c1, c2, s1;

    halfadder ha0(
        .a(ain), .b(bin),
        .c(c1), .s(s1)
    );

    halfadder ha1(
        .a(s1), .b(cin),

```

Listing 4: full adder test.sv

4

```

        end

endmodule

```

## Listing 5: 2bit

```

`timescale 1ns / 1ps
//
// //////////////////////////////////////
// Company:
// Engineer:
//
// Create Date: 09/28/2020 10:38:37 PM
// Design Name:
// Module Name: addsub3
// Project Name:
// Target Devices:
// Tool Versions:
// Description:
//
// Dependencies:
//
// Revision:
// Revision 0.01 - File Created
// Additional Comments:
//
//
// //////////////////////////////////////

module addsub3(
    input [1:0] a, b,
    input mode,
    output cbout,
    output [1:0] sout
);

    wire c1, c2;
    wire [1:0] b_n;

    assign b_n[0] = b[0] ^ mode;
    assign b_n[1] = b[1] ^ mode;

    fulladder fa0(
        .ain(a[0]) , .bin(b_n[0]), .cin(mode),
        .cout(c1), .sout(sout[0])
    );

    fulladder fa1(
        .ain(a[1]) , .bin(b_n[1]), .cin(c1),
        .cout(c2), .sout(sout[1])
    );

```

```

    assign cbout = c2 ^ mode;
endmodule

```

---

#### Listing 6: 2bit test

---

```

`timescale 1ns / 1ps
//
// //////////////////////////////////////
// Company: ELC 2137
// Engineer: Celaine Hornsby
//
// Create Date: 09/24/2020 06:14:47 PM
// Design Name:
// Module Name: addsub2_test
// Project Name:
// Target Devices:
// Tool Versions:
// Description:
//
// Dependencies:
//
// Revision:
// Revision 0.01 - File Created
// Additional Comments:
//
//
// //////////////////////////////////////

module as_test();

    reg [1:0] a;
    reg [1:0] b;
    reg m;
    wire [1:0] s;
    wire cb;

    addsub3 as(
        .a(a), .b(b), .mode(m),
        .sout(s), .cbout(cb)
    );

    initial begin

        a[0] = 0; b[0] = 1; a[1] = 0; b[1] = 0; m = 0; #10;
        a[0] = 0; b[0] = 0; a[1] = 0; b[1] = 1; m = 0; #10;
        a[0] = 0; b[0] = 1; a[1] = 0; b[1] = 1; m = 0; #10;
        a[0] = 1; b[0] = 1; a[1] = 0; b[1] = 0; m = 0; #10;
        a[0] = 0; b[0] = 1; a[1] = 1; b[1] = 0; m = 0; #10;
        a[0] = 0; b[0] = 0; a[1] = 1; b[1] = 0; m = 0; #10;
        a[0] = 0; b[0] = 1; a[1] = 0; b[1] = 0; m = 1; #10;
    end

```

```

a[0] = 0; b[0] = 0; a[1] = 0; b[1] = 1; m = 1; #10;
a[0] = 0; b[0] = 1; a[1] = 0; b[1] = 1; m = 1; #10;
a[0] = 1; b[0] = 1; a[1] = 0; b[1] = 0; m = 1; #10;
a[0] = 0; b[0] = 1; a[1] = 1; b[1] = 0; m = 1; #10;
a[0] = 0; b[0] = 0; a[1] = 1; b[1] = 0; m = 1; #10;

$finish ;
end
endmodule

```

---

## Results

 


Figure 1: Half Adder Block Diagram

Time (ns):	0	10	20	30
a	0	1	0	1
b	0	0	1	1
c	0	0	0	1
s	0	1	1	0



Figure 2: Half Adder waveform and ERT

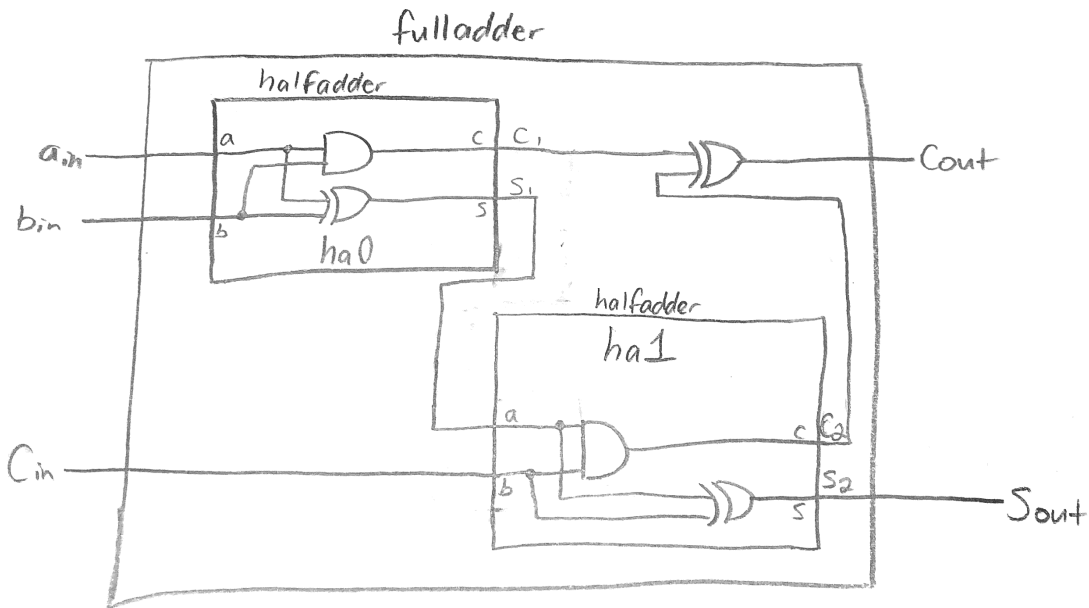


Figure 3: Full Adder Block Diagram

Time (ns):	0	10	20	30	40	50	60	70
a	0	1	0	1	0	1	0	1
b	0	0	1	1	0	0	1	1
cin	0	0	0	0	1	1	1	1
cout	0	0	0	1	0	1	1	1
sout	0	1	1	0	1	0	0	1

 


Figure 4: Full Adder Waveform and ERT



 


Figure 5: 2Bit Adder/Subtractor Block Diagram

Time (ns):	0	10	20	30	40	50	60	70	80	90	100	110
a1	0	0	0	1	0	0	0	0	0	1	0	0
b1	1	0	1	1	1	0	1	0	1	1	1	0
a2	0	0	0	0	1	1	0	0	0	0	1	1
b2	0	1	1	0	0	0	1	1	0	0	0	0
mode	0	0	0	0	0	0	1	1	1	1	1	1
c	0	0	0	0	0	0	1	1	1	0	0	0
s1	0	1	1	1	1	1	1	1	0	0	0	1
s2	1	0	1	0	1	0	1	0	1	0	1	0



Figure 6: 2Bit Adder SubtractorWaveform and ERT